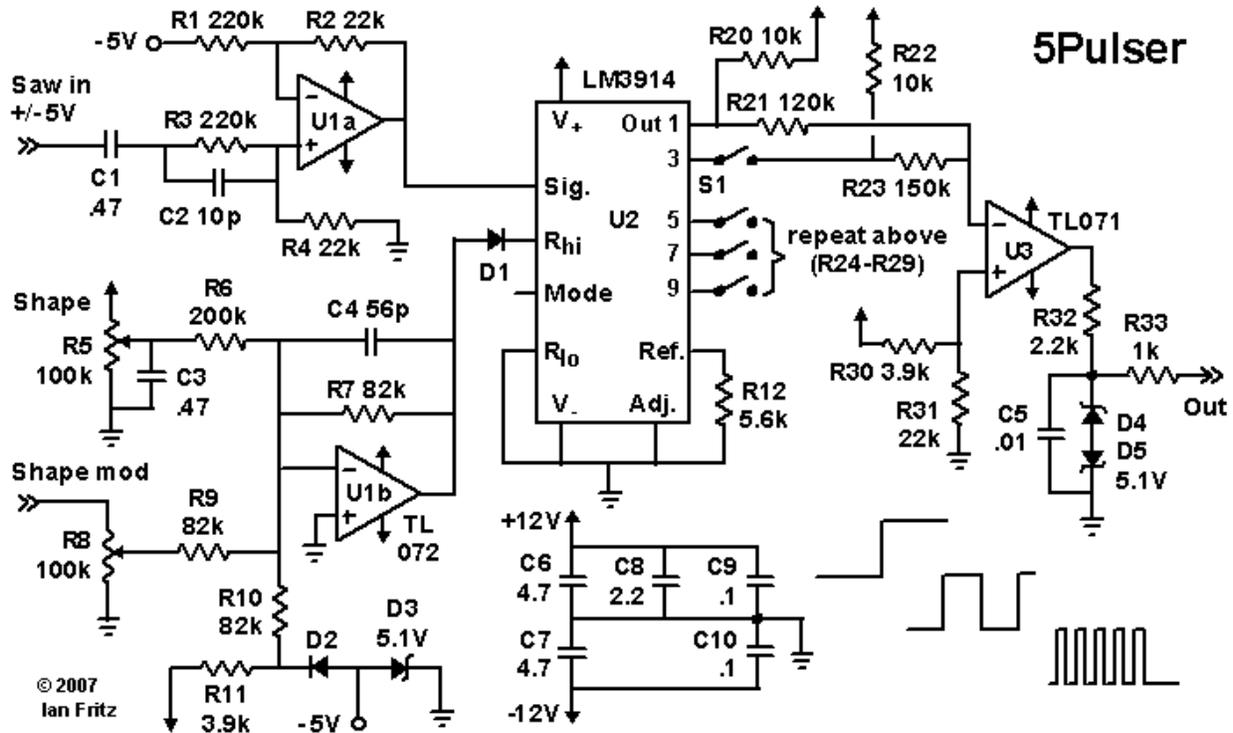


5Pulser Waveshaping Circuit

Ian Fritz, June 2007

This circuit is a voltage-controlled waveshaper that produces a train of output pulses that may be varied in number, width and position in response to a control voltage. When fed with a sawtooth waveform, the pulses evolve from a single square wave to a train of five pulses occupying half a period or less of the output waveform. The circuit is built around a LM3914 LED display driver chip, which simplifies the design of the pulse generation circuitry.

Schematic:



Component List:

ICs:

- U1 TL072 (or similar) dual opamp
- U2 LM3914 bar-graph driver
- U3 TL071 (or similar) single opamp

Diodes:

- D1, D2 1N4148 (or similar) switching diode
- D3, D4, D5 1N751A (or equivalent) 5.1 V Zener diode

Resistors (all metal film 5%):

- R33 1 kOhm
- R32 2.2 kOhm
- R11, R30 3.9 kOhm
- R12 5.6 kOhm
- R20, R22, R24, R26 10 kOhm
- R28 "


| | |
|--------------------|----------|
| R2, R4, R31 | 22 kOhm |
| R7, R9, R10 | 82 kOhm |
| R21 | 120 kOhm |
| R23, R25, R27, R29 | 150 kOhm |
| R6 | 200 kOhm |
| R1, R3 | 220 kOhm |

Pots:
R5, R8 100 kOhm

Caps:
C2 10 pF 10% ceramic
C4 56 pF 10% ceramic
C5 .01 uF 10% ceramic or poly
C9, C10 .1 uF ceramic or poly bypass
C1, C3 .47 uF poly
C8 2.2 uF electrolytic bypass
C6, C7 4.7 uF electrolytic bypass

Circuit Board:

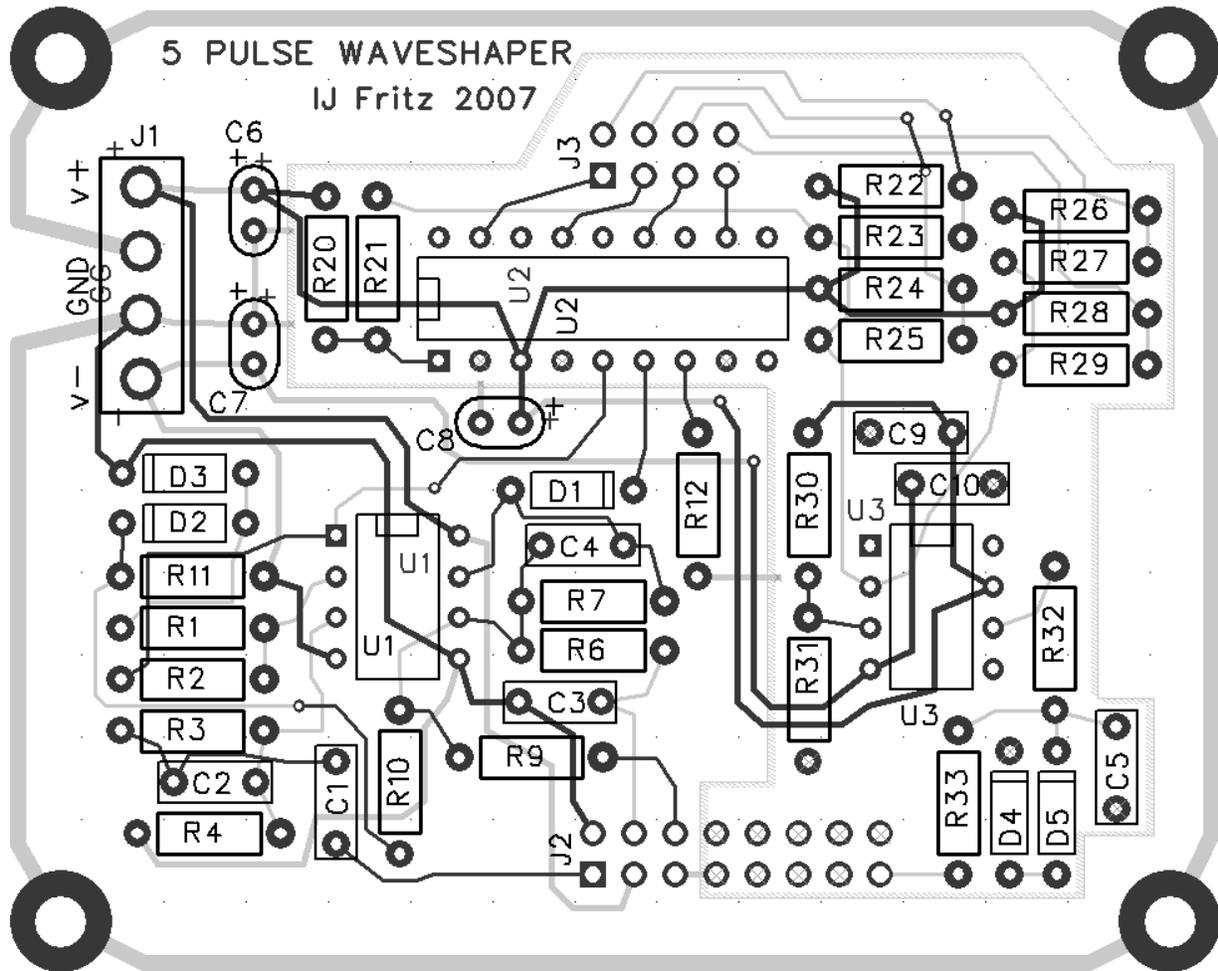The board is double sided with overall dimensions of 3.0" x 2.4". The mounting holes are spaced by 2.7" and 2.1". Component placement is indicated on the following drawing:



I/O Connector J2 Pinout:

| Pin# | Connection | Pin# | Connection |
|-------------|-------------------|-------------|---------------------------|
| 1 | Sig. in (+/- 5 V) | 2 | Gnd (Twist with Sig. in) |
| 3 | +12 V: R5(1) | 4 | Shape: R5(2) |
| 5 | Gnd: R5(3), R8(3) | 6 | Mod: R8(2) |
| 7 | Gnd | 8 | Gnd |
| 9 | Gnd | 10 | Gnd |
| 11 | Gnd | 12 | Gnd |
| 13 | Gnd | 14 | Gnd |
| 15 | Sig. out | 16 | Gnd (Twist with Sig. out) |

Note: On pots, (1) is CW, (2) is slider, (3) is CCW

Switch/Jumper J3 Pinout:

| Pin# | Connection | Pin# | Connection |
|-------------|-------------------|-------------|--------------------------|
| 1 | S1 send | 2 | S1 retn. (Or jumper 1-2) |
| 3 | S2 send | 4 | S2 retn. (Or jumper 3-4) |
| 5 | S3 send | 6 | S3 retn. (Or jumper 5-6) |
| 7 | S4 send | 8 | S4 retn. (Or jumper 7-8) |

Notes:

- 1.) Power: The circuit was developed with +/-12 V supplies. +/-15 V should work fine also, and in this case R6 should be increased to 220 k.
- 2.) The input and output leads to the panel should be twisted pairs (sig. and gnd.), as indicated in the J1 pinout chart.
- 3.) The switches S1-S4 allow different combinations of pulses to be used. These may be replaced with fixed jumper wires for operation with all five pulses.